

# Lab 5: Verilog Language

**1/ Read the following structures from Exercises carefully**

**2/ Using Verilog to implement all Exercises**

**3/ Compose testbench as unit tests to cover main functions for every Exercise**


**→ Note: At least 20 test cases for every structures**

**→ Note: Exercise 06 and 07 only need one test case → Endeavor presenting waveform**

*4/ Students can refer three examples firstly to master how to compose source code, testbench as well as simulated environment*

# Exercise 01

 1. **Requirement:** Develop the following hardware (for every figure) with Verilog HDL



a) Circuit

$s_2$	$s_1$	$s_0$	$m$
0	0	0	$u$
0	0	1	$v$
0	1	0	$w$
0	1	1	$x$
1	0	0	$y$
1	0	1	$y$
1	1	0	$y$
1	1	1	$y$

 


Figure 1.1 Multiplexer 5-1

 


Figure 1.2 Ex\_01 Design

# Exercise 02

1. **Requirement:** Develop the following hardware with Verilog HDL

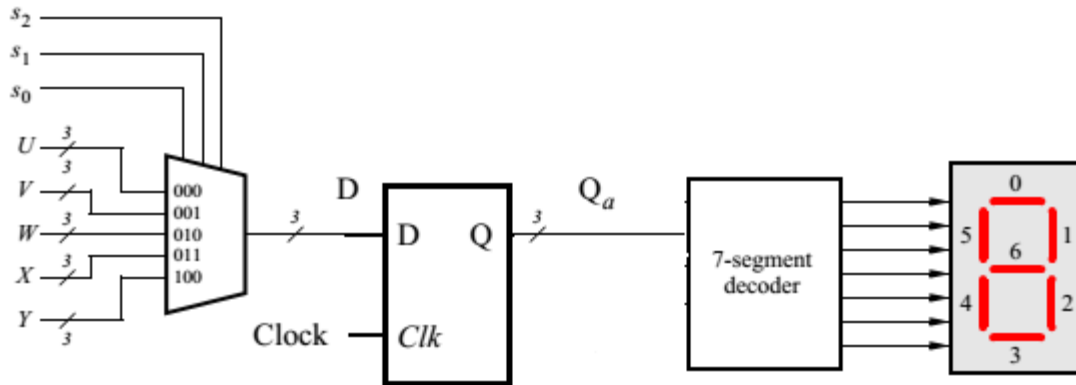


Figure 2.1 Ex\_02 Design

# Exercise 03

1. **Requirement:** Develop the following hardware with Verilog HDL

 


Figure 3.1 Ex\_03 Design

Input: ena, clk, rst\_n

Output: trigger

# Exercise 04

1. **Requirement:** Develop the following hardware (4 bit Addition) with Verilog HDL

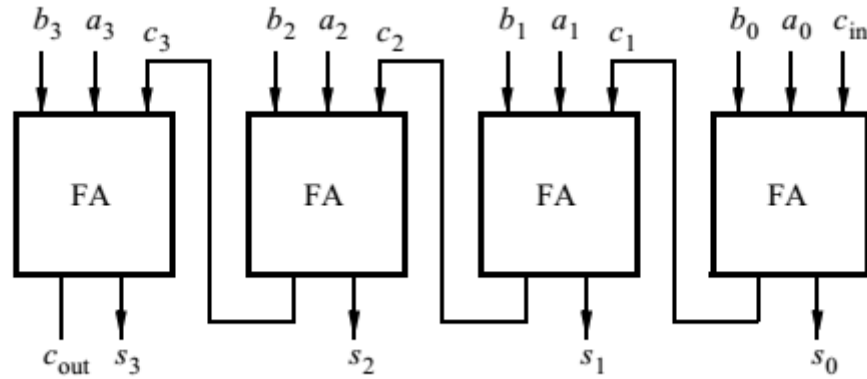


Figure 4.1 Ex\_04 Design

# Exercise 05

1. **Requirement:** Develop the following hardware (4 bit Multiplier) with Verilog HDL

 


Figure 5.1 Ex\_05 Design

# Exercise 06

1. **Requirement:** Develop the following hardware (Simple State Machine) with Verilog HDL

 


Figure 6.1 Ex\_06 Design

# Exercise 07

1. **Requirement:** Develop the following hardware (Complicated State Machine) with Verilog HDL

 


Figure 7.1 Ex\_07 Design